

# Lesson 5: Window Comparators

ET 438b Sequential Control and Data Acquisition

Department of Technology

Lesson 5\_et438b.pptx

1

## Learning Objectives


After this presentation you will be able to:

- Explain how a window comparator operates
- Construct a window comparator using OP AMPS
- Use a window comparator to detect voltages in three ranges
- Design a window comparator given values of upper and lower trip voltages.

Lesson 5\_et438b.pptx


2

## Window Comparators

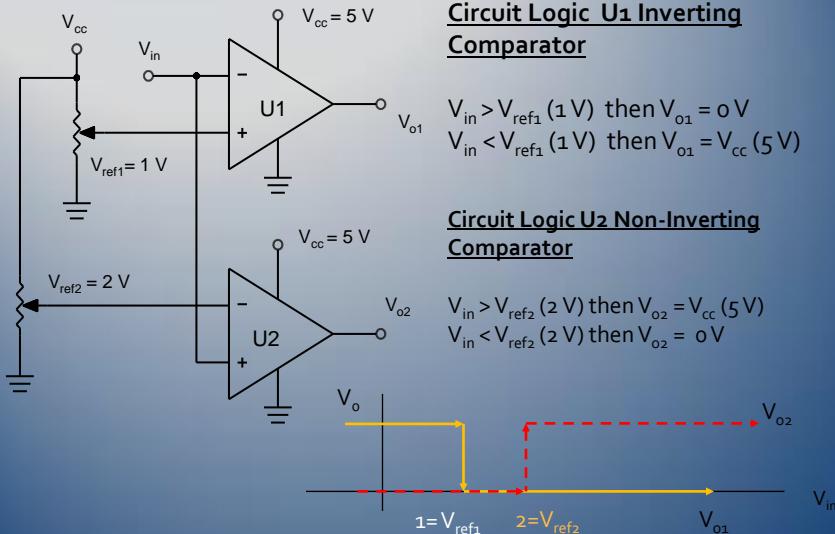
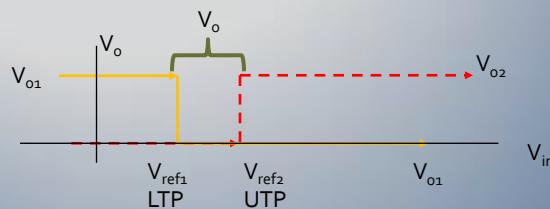
## Window Comparators



Add outputs through logic gates to get final  $V_o$ . Assume  $V_{cc} = 5$



$V_{o1}$	$V_{o2}$	$V_o$	
0	0	5	when $LTP < V_{in} < UTP$
0	5	0	when $V_{in} > UTP$
5	0	0	when $V_{in} < LTP$
5	5	0	this case never happens


Same logic as NOR gate.



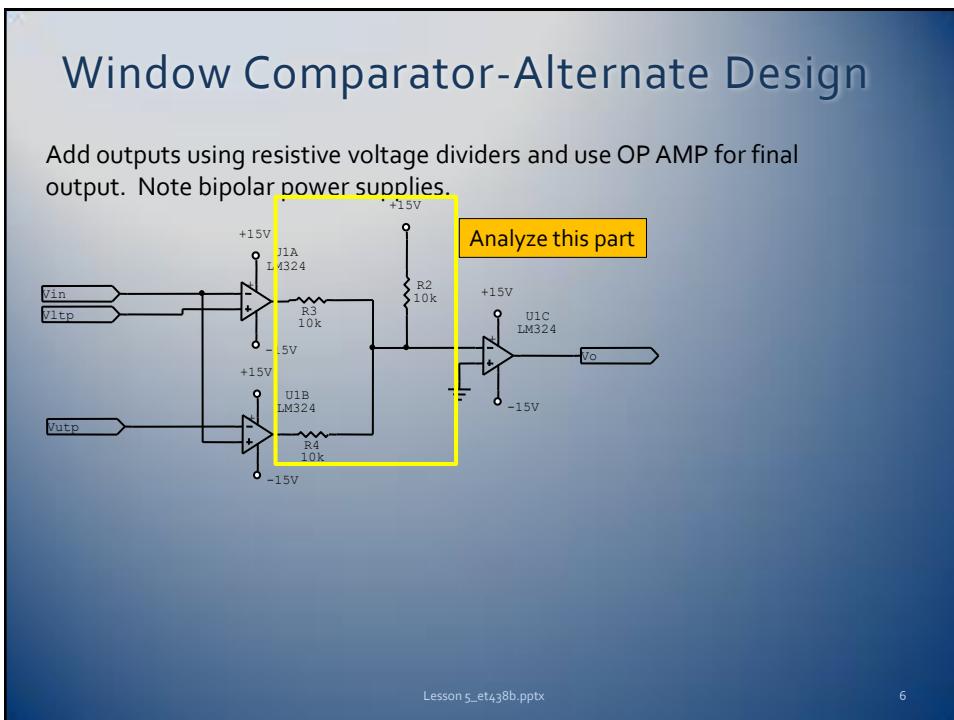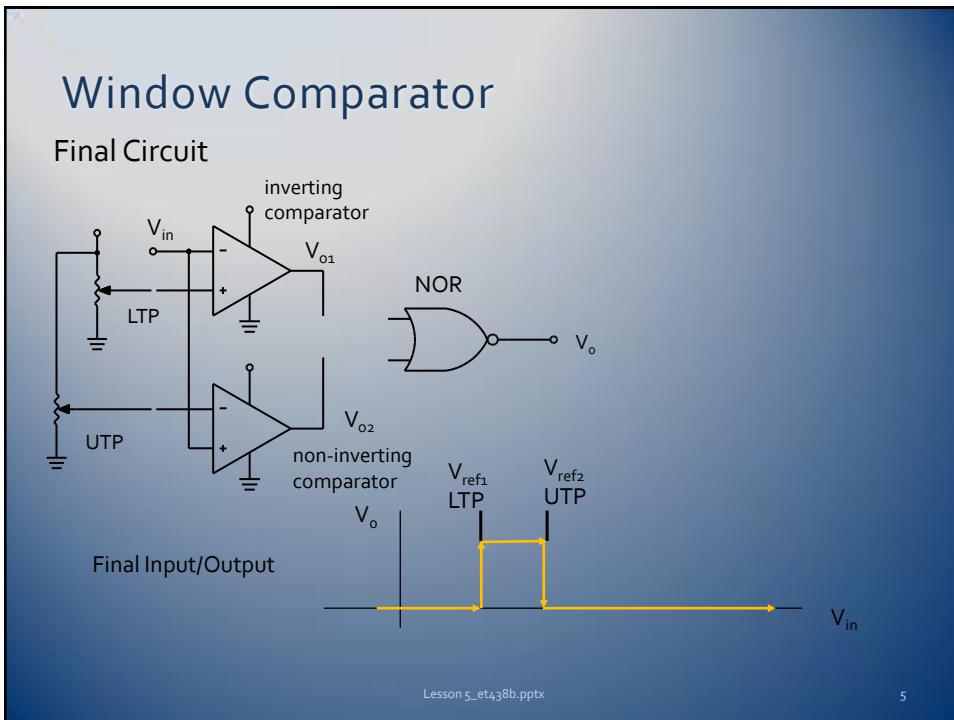


# Window Comparator-Alternate Design Analysis

Circuit enclosed

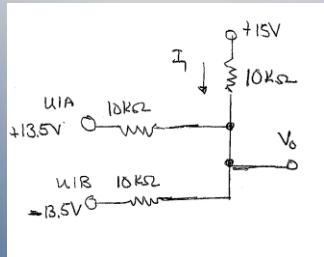


Must use superposition

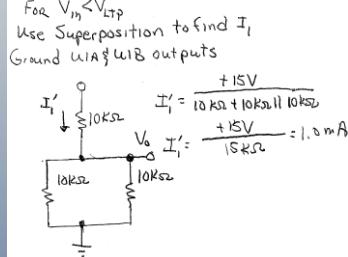

Find Contribution from U1A output  
Total current  $I'_T = 1.0\text{mA}$  from above calculations
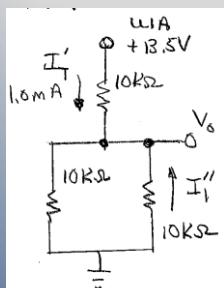
# Window Comparator-Alternate Design Analysis




$$I''_1 = -1.0\text{mA} \left[ \frac{10\text{k}\Omega}{10\text{k}\Omega + 10\text{k}\Omega} \right] = (-1.0\text{mA})(0.5)$$

$$I''_1 = -0.5\text{mA}$$

Find Contribution from U1B output (-13.5V)  
 $I'_T = 1.0\text{mA}$  from analysis above  
 $I'_T$  pos. due to flow in same direction as assumed  $I_1$
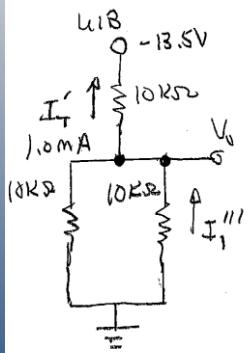
## Window Comparator-Alternate Design Analysis




$$\begin{aligned}
 I_1''' &= (1.0 \text{ mA}) \left[ \frac{10\text{k}\Omega}{10\text{k}\Omega + 10\text{k}\Omega} \right] \\
 I_1''' &= (1.0 \text{ mA})(0.5) = 0.5 \text{ mA} \\
 \text{Find } I_T & \quad I_T = I_1' + I_2'' + I_3''' = 1.0 \text{ mA} - 0.5 \text{ mA} + 0.5 \text{ mA} \\
 I_T &= 1.0 \text{ mA} \\
 \text{Find drop from } +15 \text{V supply to } V_o & \quad \text{when } V_{in} < V_{LTP} \\
 V_o &= +15 - (1 \text{ mA})(10 \text{k}\Omega) = 15 - 10 = +5 \text{Vdc}
 \end{aligned}$$

Lesson 5\_et438b.pptx

9
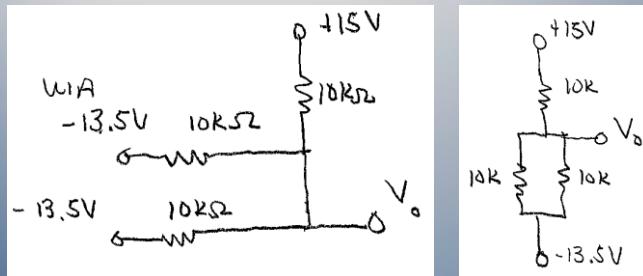
## Window Comparator-Alternate Design Analysis

For  $V_{LTP} < V_{in} < V_{UTP}$  the following circuit applies





This can be further reduced

Lesson 5\_et438b.pptx

10
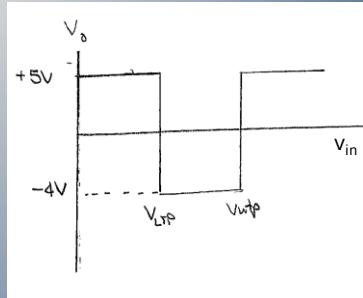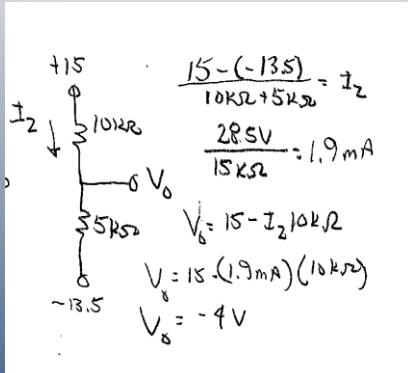
## Window Comparator-Alternate Design Analysis




Lesson 5\_et438b.pptx

11
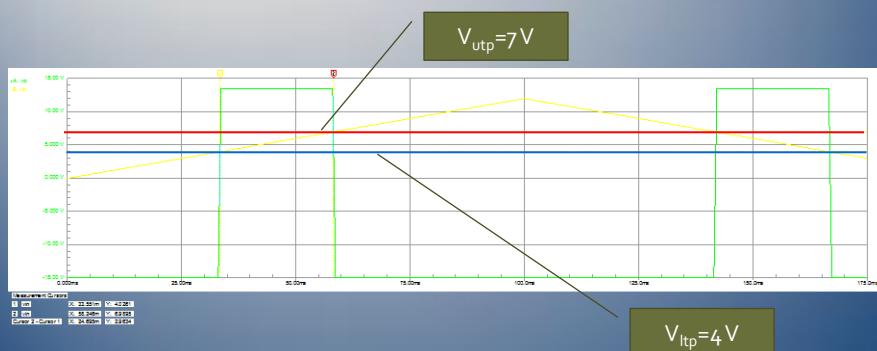
## Window Comparator Simulation

Simulation of previous circuit using piece-wise linear input and transient analysis. Uses LM 324 Quad OP AMP. (4 in 1 package)



Lesson 5\_et438b.pptx

12

## Design Example


Design a circuit that will light one of three LEDs when the output from a pressure sensor that has a gain of  $.25 \text{ V/psi}$  is connected to its input. The output should follow the specification listed below

Range	LED1	LED2	LED3
0 - 5 psi	on	off	off
5 - 10 psi	off	on	off
10 - 15 psi	off	off	on

Assume there is a 5Vdc power supply available and that all inputs and output are TTL compatible
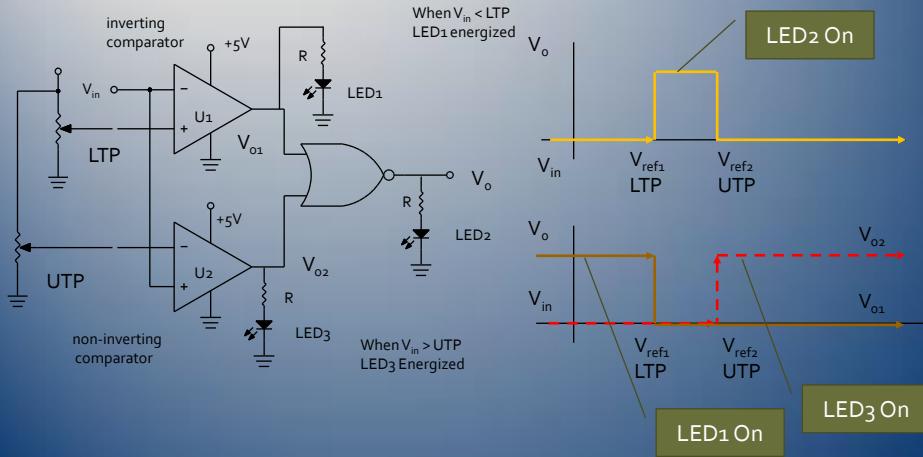
## Design Example

**Solution:** Use window comparator with LEDs connected to the outputs of each device in the circuit.



## Design Example (Continued)

Determine the values of UTP and LTP from the pressure sensor gain.

Ranges  
0 - 5 psi  
5 - 10 psi  
10 - 15 psi


$$V_{LTP} = 5 \cdot (0.25 \text{ V/psi}) = 1.25 \text{ V}$$

$$V_{UTP} = 10 \cdot (0.25 \text{ V/psi}) = 2.5 \text{ V}$$

Size resistors for LED current limiting. Determine the maximum current sourcing ability of the comparators.  
(assume 25 mA) Forward voltage drop of LEDs  $V_f = 1.2 \text{ V}$

$V_{sat}$  of U1, U2 -0.8V<sub>cc</sub>=4 V at high output
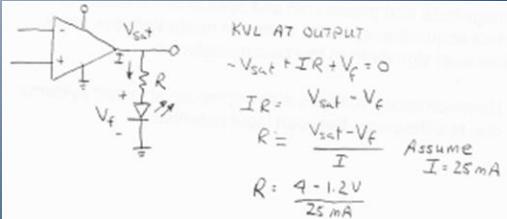
$$\text{MIN } R = 112 \Omega \quad R > 112 \Omega \quad \text{give Less than rated } I$$



Lesson 5\_et438b.pptx

15

## End Lesson 5: Window Comparators

ET 438b Sequential Control and Data Acquisition

Department of Technology

Lesson 5\_et438b.pptx

16