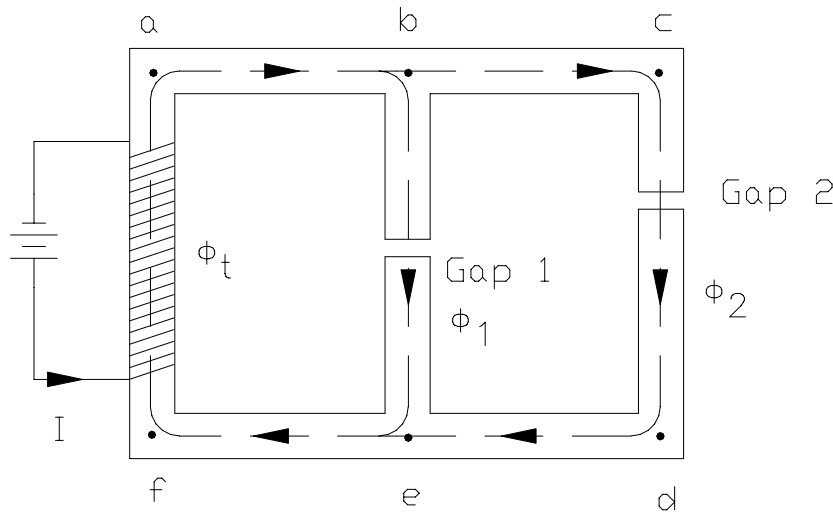


ET 332a
Magnetic Circuits Solution Using Circuits Concepts

Solve the magnetic circuit below using the electric circuits analogies. The total flux in the circuit, Φ_t is 0.012 Wb. The reluctances for the various parts of the magnetic circuit are listed below.



- $R_{\text{gap1}} = 99,500 \text{ A-t/Wb}$
- $R_{\text{gap2}} = 198,000 \text{ A-t/Wb}$
- $R_{\text{be}} = 4,630 \text{ A-t/Wb}$
- $R_{\text{abef}} = 6,400 \text{ A-t/Wb}$
- $R_{\text{bcde}} = 23,800 \text{ A-t/Wb}$

The coil has 1000 turns

1.) Draw the electrical analog schematic of the magnetic circuit shown and place the correct reluctance values on the diagram.

- 2.) Find the current, I , required in the coil to product the total flux.
- 3.) Find the flux in air gap 2.