

Lesson 14: Starting Dc Motors

ET 332a
Dc Motors, Generators and Energy Conversion
Devices

Lesson 14 332a.pptx

1

Learning Objectives

- Explain why high armature currents are present when starting a dc motor
- List the types of dc motor starting given in the presentation
- Explain how high starting currents can damage a dc motor
- Compute the value of resistance to limit motor starting current to a specified value

Lesson 14 332a.pptx

2

Starting Separately Excited and Shunt Dc Motors– Resistor Dc Motor Starters

Blocked or locked rotor current depends on E_a and R_a

$$I_a = \frac{V_T - E_a}{R_a}$$

At start-up, $E_a = 0$
since $n = 0$ so,

$$I_{as} = \frac{V_T - 0}{R_a} = \frac{V_T}{R_a}$$

R_a low to minimize losses
so I_a high at start

Dc motor starting methods:

- 1.) reduced armature voltage
- 2.) reduced current through starting resistors


Lesson 14 332a.pptx

3

Resistor Dc Motor Starters

In drawing below: R_1, R_2, R_3 sized to limit I_a to 150–200% rated.

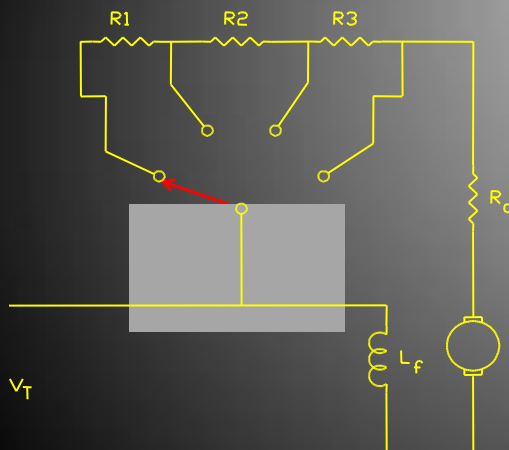Resistance values switched out as armature speed increases



Damage due to high armature current:

- 1.) brush/commutator burning
- 2.) mechanical damage due to high torques. $T \propto I_a$

Lesson 14 332a.pptx

4

Example 14-1: Motor Resistive Motor Starter

A 15 hp 230 V, 1750 rpm shunt motor has a terminal current of 56.2 A when delivering rated power at rated speed. The total armature circuit resistance, R_a , is 0.28 ohms and the field resistance, R_f , is 137 ohms. Compute:

- 1.) rated torque at the shaft (N-m)
- 2.) armature current for a locked rotor
- 3.) the value of external resistance required to limit I_a and developed torque to 200% of rated.
- 4.) the locked rotor torque when the terminal voltage drops to 215 V and the starting resistor is used to limit the armature current.

Lesson 14 332a.pptx

5

Example 14-1 Solution (1)

Part (1)

$$P_o = (746 \text{ W/hp})(15 \text{ hp}) = 11,190 \text{ W}$$

$$\omega = 1750 \text{ rpm} \left[\frac{2\pi}{60} \right] = 183.167 \text{ rad/s}$$

$$T_{\text{rated}} = \frac{P_o}{\omega} = \frac{11,190 \text{ W}}{183.167 \text{ rad/s}} = \boxed{61.1 \text{ N-m}}$$

Part (2)

At start-up $E_a = 0$ $n = 0$ $R_{\text{acir}} = 0.28 \Omega$

Starting current

$$I_{\text{as}} = \frac{V_T}{R_{\text{acir}}}$$

Compare to rated current

$$I_{\text{as}} = \frac{230 \text{ V}}{0.28 \Omega} \quad \frac{I_{\text{as}}}{I_T} = \frac{821.43 \text{ A}}{56.2 \text{ A}} = 14.62 \times \text{rated}$$

$$I_{\text{as}} = 821.43 \text{ A}$$

Lesson 14 332a.pptx

6

Example 14-1 Solution (2)

Part (3)

I_{a1} = armature I at rated output

I_{a2} = armature I at 200% rated torque

T_1 = Rated T

T_2 = 200% rated T

$$I_{a1} = I_T - I_f$$

$$I_{a1} = 56.2A - \frac{230V}{137\Omega}$$

$$I_{a1} = 54.52A$$

Torque proportional to I_a so

$$T_1 = K_T I_{a1} \quad T_2 = K_T I_{a2}$$

$$\frac{T_1}{T_2} = \frac{K_T I_{a1}}{K_T I_{a2}} \quad \text{solve for } I_{a2}$$

$$\frac{T_1}{T_2} = \frac{I_{a1}}{I_{a2}} \quad T_2 = 2T_1$$

Lesson 14 332a.pptx

7

Example 14-1 Solution (3)

$$\frac{T_1}{2T_1} = \frac{54.52A}{I_{a2}} \Rightarrow I_{a2} = 109.04A$$

← Answer

$I_{a1} = 54.52A$

Find the value of the current limiting Resistance, R_x

$$V_T = E_a + I_{a2}(R_{acir} + R_x) \quad \frac{V_T}{I_{a2}} = R_{acir} + R_x$$

$E_a = 0 \quad n = 0$

$$R_x = \frac{V_T}{I_{a2}} - R_{acir} \quad R_x = \frac{230V}{109.04A} - 0.28\Omega$$

← Answer

$$R_x = 1.83\Omega$$

Lesson 14 332a.pptx

8

Example 14-1 Solution (4)

Part (4)

Assume no saturation, V_T reduced to 215 V, which reduces field current and flux. Compute new I_f .

$$I_f = \frac{215V}{137\Omega} = 1.57A \quad \text{Calculate } I_{as} \text{ with reduced } V_T$$

$$I_{as} = \frac{V_T}{R_{ac1q} + R_x} = \frac{215V}{0.28 + 1.83\Omega}$$

$$I_{as} = 101.9A$$

Remember $T \propto I_a I_f$

Assume linear magnetic circuit

$$\frac{T_{230}}{T_{215}} = \frac{[I_f I_a]_{230}}{[I_f I_a]_{215}}$$

Lesson 14 332a.pptx

9

Example 14-1 Solution (5)

Solve for new torque at 215 V

$$T_{215} = \left[\frac{[I_f I_a]_{215}}{[I_f I_a]_{230}} \right] T_{230}$$

$$T_{215} = \left[\frac{(1.57A)(101.9A)}{(1.68A)(54.52A)} \right] 1.09 \text{ N}\cdot\text{m}$$

$$T_{215} = 106.7 \text{ N}\cdot\text{m}$$

Answer

Less than 200%

Lesson 14 332a.pptx

10

End Lesson 14

» ET 332a
Dc Motors, Generators and
Energy Conversion Devices