

Lesson 24: Photocell Electrical Characteristic and Circuit Model

ET 332a
Dc Motors, Generators and Energy Conversion Devices

1

Lesson 24 332a.pptx

Learning Objectives


After this presentation you will be able to:

- Identify and interpret a photocell electrical characteristic
- Find the maximum power output from a photocell
- Calculate a photocell's efficiency
- Determine circuit model parameters for a photocell given its characteristic curve
- Perform a calculation using the circuit model of a photocell.

▶ 2

Lesson 24 332a.pptx

Photocell Characteristic Curve

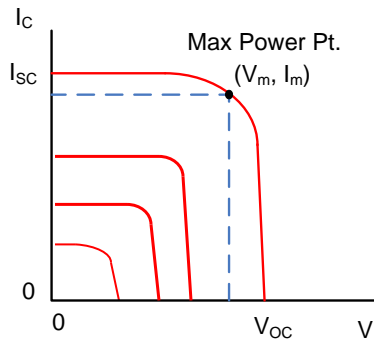

P_m = Maximum cell power

Fill Factor = FF

$$P_M = I_M V_M$$

$$FF = \frac{P_m}{I_{SC} V_{OC}}$$

0.7 < FF < 0.85 Typical FF range

Cell Efficiency $\eta_C = \frac{P_C}{P_I}$

P_I = incident solar power

▶ 3

Lesson 24 332a.pptx

Solar Cell Characteristics Example (1)

Example: A photocell has a saturation current of 2.5×10^{-12} A and a short circuit current of 35 mA. It has an area of 1.5 cm^2 . The incident solar power is 1000 W/m^2 . Assume that the cell operates at room temperature. Find V_{OC} , P_m , Fill Factor and conversion efficiency.

$$I_S := 2.5 \cdot 10^{-12} \text{ A}$$

$$I_{SC} := 0.035 \text{ A}$$

$$V_T := 0.026 \text{ V}$$

$$I_L := I_{SC}$$

$$V_{OC} := V_T \cdot \ln \left(1 + \frac{I_L}{I_S} \right)$$

$$V_{OC} = 0.607 \text{ V}$$

▶ 4

Lesson 24 332a.pptx

Solar Cell Characteristics Example (2)

Find P_m graphically

Create function for plotting

$$I_c(V) := I_L - I_s \cdot \left(e^{\frac{V}{V_T}} - 1 \right)$$

Define plot range

$$V := 0.0, 0.02.. 0.62 \quad V$$


Calculate power as function of V

$$P(V) := I_c(V) \cdot V \quad W$$

▶ 5

Lesson 24 332a.pptx

Solar Cell Characteristics Example (3)

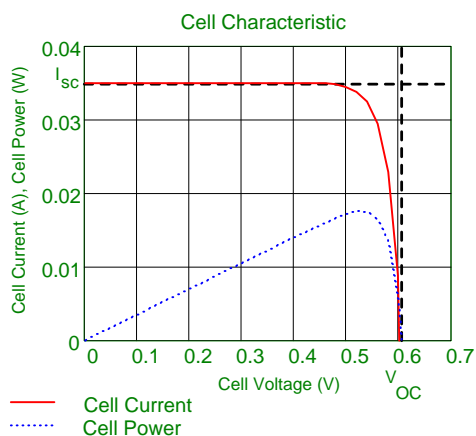

$$V_m := 0.5360 \quad V \quad P_m := 0.0177 \quad W$$

$$I_m := I_c(V_m) \quad I_m = 0.0328 \quad A$$

Find the Fill Factor (FF)

$$FF := \frac{P_m}{V_{OC} \cdot I_{sc}} \quad FF = 0.8$$

▶ 6

Lesson 24 332a.pptx

Solar Cell Characteristics Example (4)

Find the cell efficiency at maximum power output

Find the incident power, P_I

$$I := 1000 \cdot \frac{\text{W}}{\text{m}^2} \quad A := 1.5 \cdot \text{cm}^2$$

$$A_m := A \cdot \frac{1 \cdot \text{m}^2}{10000 \cdot \text{cm}^2} \quad A_m = 1.5 \times 10^{-4} \text{m}^2$$


$$P_I := A_m \cdot I \quad P_I = 0.15 \text{W} \quad P_m := 0.0177 \cdot \text{W}$$

$$\eta_C := \frac{P_m}{P_I} \quad \eta_C = 0.1 \quad \text{Cell efficiency is 10\%}$$

▶ 7

Lesson 24 332a.pptx


Circuit Model of Solar Cell

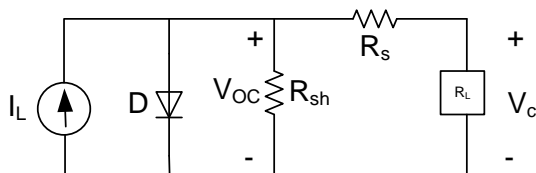

R_s slope of characteristic near V_{OC}

R_{sh} slope of characteristic near I_{sc}


Values determined by cell construction

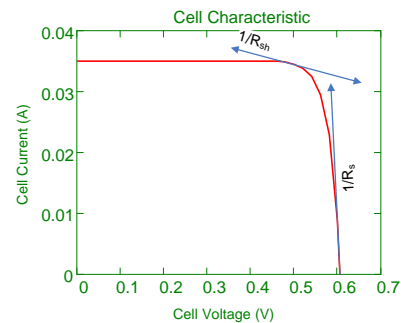

▶ 8

Lesson 24 332a.pptx

Solar Cell Circuit Model Parameters

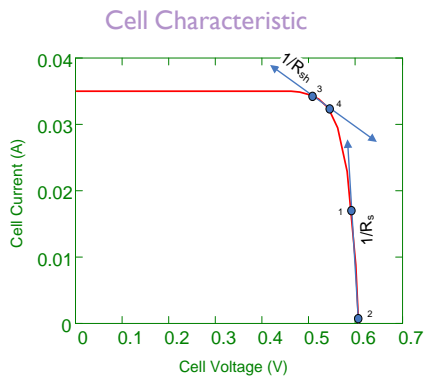

Finding Model Parameters, R_{sh} and R_s

Pick points on characteristic plot and compute slope.

For R_s use points 1 and 2.

$$1.) \quad V_{1s} := 0.5781 \text{ V} \quad I_{1s} := 0.02395 \text{ A}$$

$$2.) \quad V_{2s} := 0.6058 \text{ V} \quad I_{2s} := 3.9 \cdot 10^{-4} \text{ A}$$

$$G_s := \frac{I_{2s} - I_{1s}}{V_{2s} - V_{1s}} \quad \text{Conductance is } 1/R_s$$

$$R_s := \frac{1}{G_s} \quad G_s = 0.8505 \text{ S} \quad R_s = 1.176 \text{ } \Omega$$

For R_{sh} use points 3 and 4

$$3.) \quad V_{1sh} := 0.512 \text{ V} \quad I_{1sh} := 0.0343 \text{ A}$$

$$4.) \quad V_{2sh} := 0.550 \text{ V} \quad I_{2sh} := 0.0311 \text{ A}$$


$$G_{sh} := \frac{I_{2sh} - I_{1sh}}{V_{2sh} - V_{1sh}} \quad \text{Conductance is } 1/R_{sh}$$

$$R_{sh} := \frac{1}{G_{sh}} \quad G_{sh} = 0.0842 \text{ S} \quad R_{sh} = 11.875 \text{ } \Omega$$

▶ 9

Lesson 24 332a.pptx

Solar Cell Circuit Model Example (1)

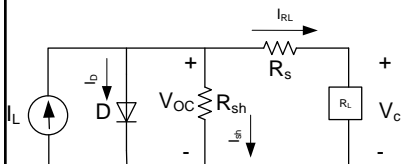

Example: Find the power delivered to a 30 ohm resistive load by the solar cell with a light current of 100 mA and model parameters of $R_s = 1.176 \text{ } \Omega$ and $R_{sh} = 11.875 \text{ } \Omega$. Determine the cell load voltage for this load resistance.

$$I_L := 100 \cdot \text{mA} \quad V_{OC} := 0.71 \cdot \text{volt}$$


$$R_{sh} := 11.875 \cdot \Omega \quad R_s := 1.176 \cdot \Omega \quad R_L := 30 \cdot \Omega$$

$$\text{By KCL} \quad I_L - I_D - I_{eq} = 0$$

$$R_{eq} := \frac{(R_s + R_L) \cdot R_{sh}}{(R_s + R_L) + R_{sh}} \quad R_{eq} = 8.599 \text{ } \Omega$$

$$\text{Parallel circuit so.....} \quad I_{eq} := \frac{V_{OC}}{R_{eq}} \quad I_{eq} = 82.6 \text{ mA}$$

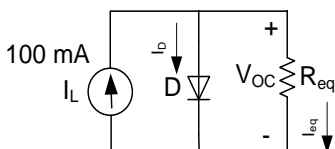
$$I_D := I_L - I_{eq} \quad I_D = 17.4 \text{ mA}$$



▶ 10

Lesson 24 332a.pptx

Solar Cell Model Example (2)

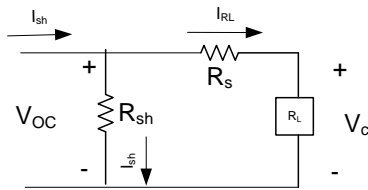

Use Current Divider rule to find I_{RL}

$$I_{RL} := I_{eq} \cdot \frac{R_{sh}}{R_{sh} + (R_L + R_s)} \quad I_{RL} = 22.77 \text{ mA}$$

$$P_L := I_{RL}^2 \cdot R_L \quad P_L = 15.6 \text{ mW}$$

Find V_C from KVL $V_C := V_{OC} - I_{RL} \cdot R_s$

$$V_C = 0.683 \text{ V}$$

▶ 11

Lesson 24 332a.pptx

Solar Cell Efficiency

- ▶ AM1.5 Solar Intensity (Incident power density) 1000 W/m^2 or 100 W/cm^2
- ▶ Losses
 - ▶ Photon Energy -47% of photons have $eV < 1.1$, 30% goes to heat
 - ▶ Voltage factor – ratio of energy given to energy required to produce electron 0.65
 - ▶ Recombination – electron/holes that recombine 10%
 - ▶ Reflection – reduced to 4%
 - ▶ Overall Efficiency $\eta_c = (0.47)(0.65)(1-0.10)(.96) = .26$
 - 26% Maximum efficiency using current technologies

▶ 12

Lesson 24 332a.pptx

End Lesson 24

ET 332a

Dc Motors, Generators and Energy Conversion Devices