

Lesson 8: Induced Voltage in Practical dc Machines

ET 332a

Dc Motors, Generators and Energy Conversion Devices

1

Learning Objectives

After this presentation you will be able to:

- Compute the average output voltage of a dc generator given machine physical construction parameters.
- Draw the schematic circuit model of a dc machine
- Find generator output voltage using a magnetization curve and defining formulas.
- Compute generator voltage regulation.

2

Average Induced Voltage in a Generator

Start with fundamental equation

$$e = B \cdot l \cdot v \cdot \sin(\theta)$$

Where v = velocity of conductor

For rotating system

$$v = \text{angular velocity } d\theta/dt = \omega \text{ rad/s}$$

Angular velocity relates to frequency f (cycles/s or Hertz) by: $\omega = 2\pi f$

Frequency of e related to number of field poles and rotational speed by:

$$f = \frac{P \cdot n}{120}$$

Where: P = number of field poles
 n = rotational speed (rpm)

3

Average Induced Voltage in a Generator

Substituting into fundamental equation and simplifying gives:

$$E_a = \frac{n \cdot P \cdot N_a \cdot \Phi_p}{30}$$

Where: P = number of poles

n = rotational speed

N_a = # of turns in coil

Φ_p = field flux

E_a = average induced voltage

Consider machine construction details and define another voltage formula

4

Average Induced Voltage in a Generator

Define the number of conductors in field in terms of windings

$$N_a = \frac{Z_a}{2}$$

z_a = Total number of armature conductors in the field.

Substitute into previous equation to get:

$$E_a = \frac{n \cdot P \cdot z_a \cdot \Phi_p}{60 \cdot a}$$

Where:

a = number of parallel paths

5

Average Induced Voltage in a Generator

The number of poles, parallel paths, and conductors are constant once the machine is constructed so define:

$$k_G = \frac{P \cdot z_a}{60 \cdot a} \quad \text{Where } k_G = \text{emf constant}$$

The constant k_G also known as k_e in some texts. Relates motor voltage to speed and field flux.

$$E_a = k_G \cdot n \cdot \Phi_p = k_e \cdot n \cdot \Phi_p$$

Note : E_a is proportional to the flux and to the rotational speed. If conditions of machine are know at one n and Φ_p , another operating point can be found by equating ratios.

6

Induced Voltage Examples

Example 1: A 2 pole dc motor armature rotates at 1800 rpm. It has 400 turns in the armature winding. The magnetic field flux is 0.0025 Wb. Compute the average induced voltage.

$$E_a = \frac{n \cdot P \cdot z_a \cdot \Phi_f}{60 \cdot a} = \frac{1800(2)(400)(0.0025)}{60(2)} = 125 \text{ Vdc}$$

Example 2: A 4 pole dc machine rotates at 200 rad/s in a magnetic field of 0.0048 Wb. There are 4 parallel current paths that have 200 conductors. Find the induced voltage in the armature and the emf constant for the machine.

Convert ω to n for formula $n = \left(\frac{60}{2\pi}\right) \cdot 200 \text{ rad/s} = 1910.8 \text{ rpm}$

$$E_a = \frac{n \cdot P \cdot z_a \cdot \Phi_p}{60 \cdot a} = \frac{(1910.8 \text{ rpm})(4)(200)(0.0048 \text{ Wb})}{60(4)} = 30.57 \text{ Vdc}$$

7

Induced Voltage Examples

Example 2 Continued: Find the emf constant

Lump the constants and compute

$$k_e = \frac{P \cdot z_a}{60 \cdot a} = \frac{(4)(200)}{60(4)} = 3.333 \text{ V/Wb-rpm}$$

Example 3: A 4 pole 50 kW dc machine has a value of $E_a = 110 \text{ V}$ at 1100 rpm. What is the induced voltage if the speed is increased 20%?

$E_{a1} = k_e \omega_1 \Phi_f$ $E_{a2} = k_e \omega_2 \Phi_f$ No change in flux $E_{a1} = 110 \text{ V}$ $\omega_1 = 1100 \text{ rpm}$
 $E_{a2} = k_e \omega_2 \Phi_f$ $\omega_2 = \omega_1 \cdot 1.2 = 1320 \text{ rpm}$

Find E_{a2} $\frac{E_{a1}}{E_{a2}} = \frac{k_e \omega_1 \Phi_f}{k_e \omega_2 \Phi_f} = \frac{\omega_1}{\omega_2}$ $\frac{110}{E_{a2}} = \frac{1100}{1320} \Rightarrow E_{a2} = \frac{1320}{1100} \cdot 110 = 132 \text{ Vdc}$ **Ans**

8

Induced Voltage Examples

Example 4: A 4 pole dc machine has a value of $E_a = 50$ V at 400 rpm. What is the value of E_a if the pole flux is doubled while the speed remains constant?

$$E_{a1} = k_e n_1 \Phi_{p1} \quad E_{a2} = k_e n_2 \Phi_{p2}$$

$$n_1 = n_2 \quad n_2 = 400$$

$$\Phi_{p2} = 2 \Phi_{p1}$$

$$\frac{E_{a2}}{E_{a1}} = \frac{k_e n_1 \Phi_{p2}}{k_e n_2 \Phi_{p1}} = \frac{k_e (400) 2 \Phi_{p1}}{k_e (400) \Phi_{p1}}$$


$$\frac{E_{a2}}{E_{a1}} = \frac{1}{1} \quad \rightarrow \quad E_{a2} = 1 E_{a1} \quad \text{Ans}$$

$$E_{a2} = 1(50) = 50 \text{ vdc}$$

Assumes no saturation

9

Circuit Model of Dc Machines

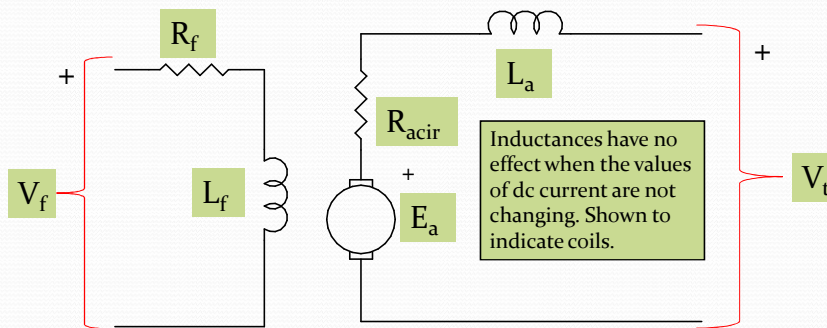


E_a = internally induced voltage
 V_t = terminal voltage of machine
 V_f = field electromagnetic source voltage

R_{acir} = dc resistance of the armature windings, interpoles, etc
 L_a = inductance of armature circuit
 R_f = dc resistance of the field windings
 L_f = inductance of the field windings

10

Generator Circuit Model

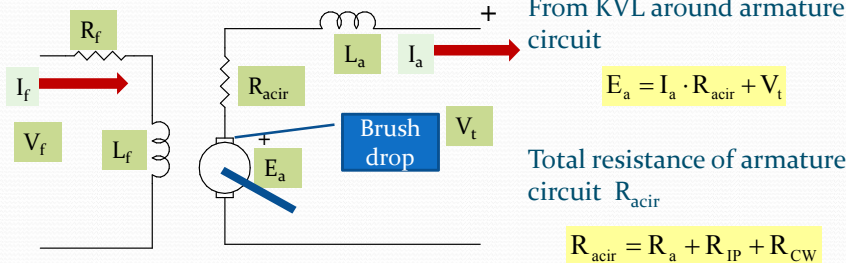

Generator model - mechanical power converted to electric power. I_a leaves the + terminal of armature


Where:
 R_a = armature resistance
 R_{IP} = interpole winding resistance
 R_{CW} = compensation winding resistance

Field current produces field flux

Brush losses $P=2 \cdot I_a$
 1 volt drop for each brush

11

Motor Circuit Model

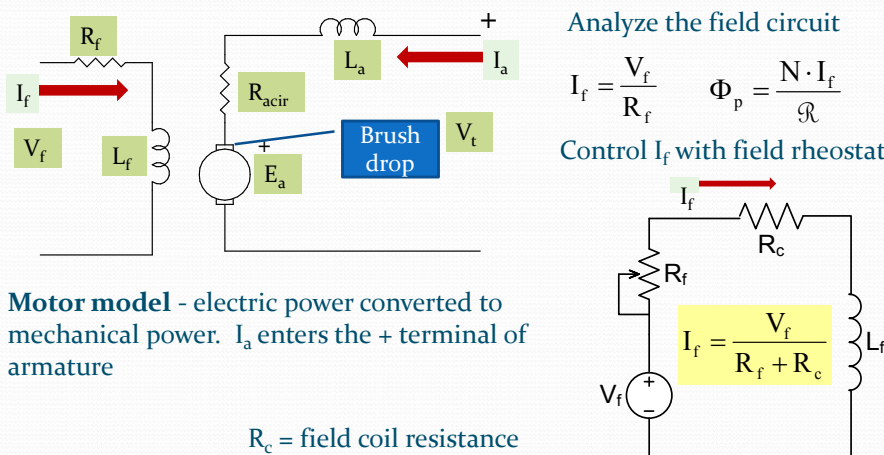


Motor model - electric power converted to mechanical power. I_a enters the + terminal of armature

12

Separately Excited Dc Generator

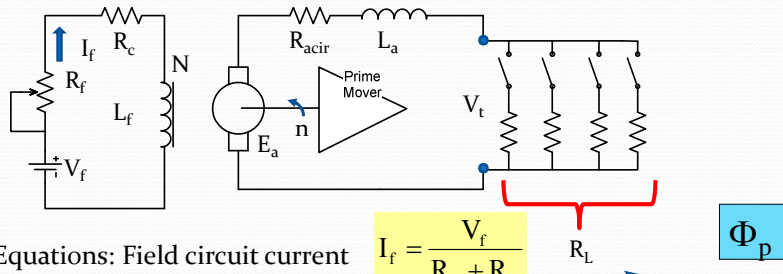Separate source of supply develops field flux. Source called the **exciter**



Model Equations: Field circuit current

$$I_f = \frac{V_f}{R_f + R_c}$$

$$\Phi_p$$

Magnetic coupling to induced average voltage

E_a in terms of flux for constant I_f

$$E_a = k_G \cdot n \cdot \Phi_p$$

$$E_a = \frac{N \cdot I_f \cdot n \cdot k_G}{\mathcal{R}}$$

$$k_e = k_G \cdot \Phi_p$$

$$E_a = k_e \cdot n$$

$$E_a \text{ proportional to } n \text{ for constant } I_f$$

13

Separately Excited Dc Generator


Generally flux, Φ is non-linear with respect to the field current I_f

Magnetizing curve for generator gives relationship for E_a as a function of field current.

If I_f is in linear part of curve E_a is proportional to n and I_f

$$E_a = k_G \cdot n \cdot \Phi_p$$


Generator Magnetizing Curve

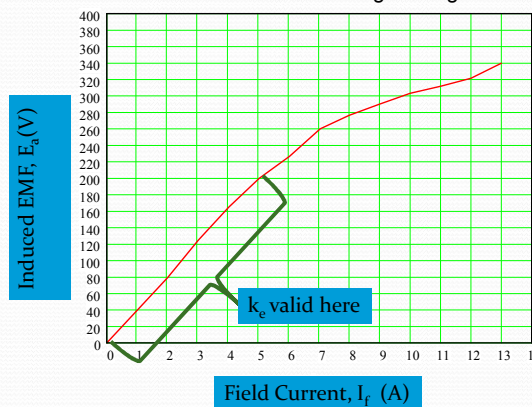

14

Terminal Voltage Regulation

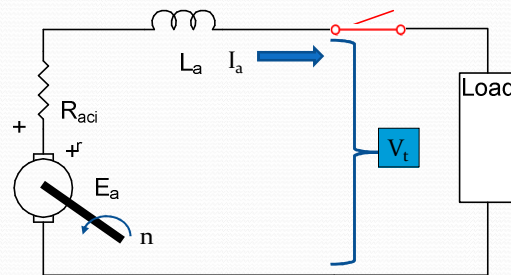Voltage regulation finds the percent change in terminal voltage from no-load to full load



KVL around armature circuit with switch closed

$$E_a = I_a \cdot R_{acir} + V_t$$

With switch closed and n constant $V_t < E_a$ and decreases as I_a increases

$I_a = 0$ with switch open so: $E_a = 0 \cdot R_{acir} + V_t$ No-load voltage = E_a
 $E_a = V_t$

15

Terminal Voltage Regulation

For rated terminal voltage

$$\%VR = \frac{V_{nl} - V_{rated}}{V_{rated}}$$

Where: %VR = percent voltage regulation

V_{nl} = no-load terminal voltage


V_{rated} = name plate rating of the terminal voltage when generator delivers rated power.

How does terminal voltage change with delivered power?

16

Terminal Voltage Regulation

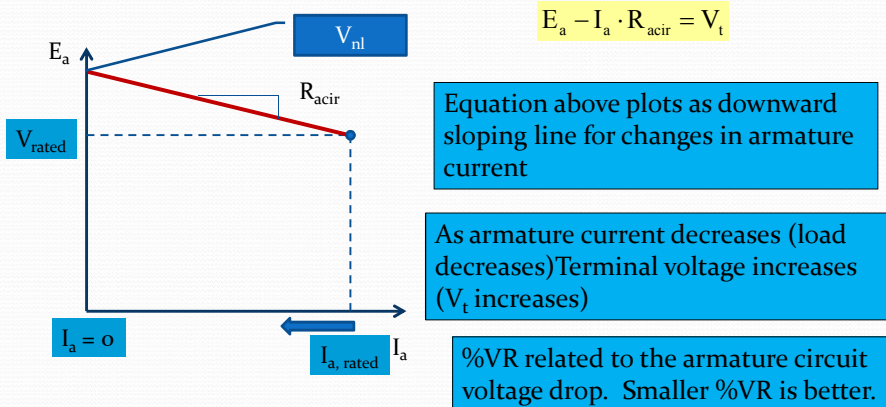Generator Terminal Voltage Vs Load Current



17

Voltage Regulation Example

Example 1 A separately excited 50 kW, 3500 rpm, 2-pole dc generator has a rated terminal voltage of 120 Vdc. Its exciter is supplied from a 120 Vdc supply. The field coil resistance is 10.4Ω and the field rheostat is set at 20.5Ω . The total armature resistance is 0.014Ω . The generator is supplying 420 A to a load. The magnetizing curve is given on a previous slide.


Determine:

- the induced armature voltage at this level of excitation
- the terminal voltage at 100%, 75% and 50% load current

18

Voltage Regulation Solution

Draw schematic model for generator

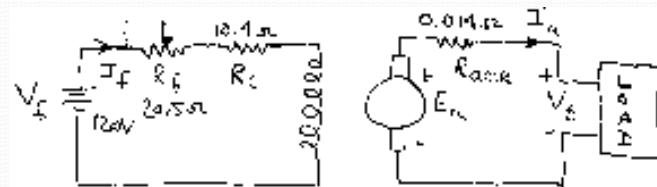

$$I_f = \frac{V_f}{R_f + R_c}$$

$$I_f = \frac{120\text{V}}{20.5\Omega + 10.4\Omega}$$

$$I_f = 3.83\text{A}$$

Use I_f and magnetization curve to find E_a

From Magnetization Curve $E_a = 162\text{V}$ at $I_f = 3.83\text{A}$

ii) $I_a = 420\text{A}$ at 75% Load

Find at terminal voltage $V_t = 162\text{V}$

$$E_a = I_a R_{a,eq} + V_t$$

$$162 - I_a R_{a,eq} = V_t$$

$$R_{a,eq} = 0.014\Omega$$

19

Voltage Regulation Solution

Solution continued: Compute regulation at different load levels

① 100% Load $162 - 420\text{A}(0.014\Omega) = V_t$
 $162 - 5.88 = V_t$
 $V_t = 156.12\text{V}$ Ans

② 75% Load $I_{a,75} = \frac{100}{75}(420\text{A}) = 315\text{A}$
 $E_a = I_{a,75} R_{a,eq} + V_t$
 $162 - 315\text{A}(0.014\Omega) = V_t$
 $V_t = 157.59\text{V}$ Ans

20

Voltage Regulation Solution

Solution continued: Compute regulation at different load levels

$$\begin{aligned}
 & \text{a) } 50\% \text{ Load} \\
 & I_{arm} = \frac{50\%}{100\%} (420 \text{ A}) \\
 & I_{arm} = 210 \text{ A} \\
 & E_a = I_{arm} R_{acir} + V_t \\
 & 142 + 210 \text{ A} (0.014 \Omega) = V_t \\
 & 142.294 \text{ V} = V_t \\
 & \text{ANS. } 15\% \text{ Reg} = \frac{V_t}{V_r}
 \end{aligned}$$

Summary of calculations

% Load	I_a	V_t
100	420 A	156.12
75	315 A	157.59 V
50	210 A	159.86 V

Terminal voltage increases on generator as the load current decreases

21

Separately Excited Generator Example

Example 2: For the machine in Example 1, determine the field rheostat setting for the machine to deliver rated output current at rated voltage. Also determine the %VR at rated load.

Solution

Calculate the current at rated load for the generator power rating

$$P_{\text{rated}} = 50 \text{ kW} = 50,000 \text{ W}$$

Find Rated I from power and voltage

$$V_{\text{rated}} = V_t = 120 \text{ V dc}$$

$$I_{a,\text{rated}} = \frac{P_{\text{rated}}}{V_t} = \frac{50,000 \text{ W}}{120 \text{ V}} = 416.7 \text{ A}$$

Now find value of E_a with $V_t = 120 \text{ V}$ using $E_a = I_a \cdot R_{acir} + V_t$

22

Separately Excited Generator Example

Example 2 Continued

$$R_{acir} = 0.014 \Omega$$

$$E_a = I_a \cdot R_{acir} + V_t$$

$$E_a = 416.7 \text{ A} \cdot (0.014 \Omega) + 120 \text{ V}$$

$$E_a = 125.833 \text{ V}$$

Use magnetization curve to find I_f $I_f = 2.8 \text{ A}$ from graph. Now find R_f

$$I_f = \frac{V_f}{R_f + R_c} \quad \text{Solve for } R_f \quad \begin{aligned} I_f(R_f + R_c) &= V_f \\ I_f R_f + I_f R_c &= V_f \end{aligned} \quad \rightarrow \quad \begin{aligned} I_f R_f &= V_f - I_f R_c \\ R_f &= \frac{V_f}{I_f} - R_c \end{aligned}$$

23

Separately Excited Generator Example

Example 2 Continued

From Previous example

$$R_f = \frac{V_f}{I_f} - R_c \quad R_c = 10.4 \Omega$$

$$R_f = \frac{120 \text{ V}}{2.8 \text{ A}} - 10.4 \Omega = 32.46 \Omega$$

Find the % VR Percent Voltage Regulation $V_{rated} = V_t = 120 \text{ V}$

$$V_{nl} = V_t \text{ with } I_a = 0 \quad E_a = I_a \cdot R_{acir} + V_t \quad \rightarrow \quad E_a = 0 \cdot R_{acir} + V_t = E_a = V_t$$

$$V_{nl} = 125.833$$

$$\%VR = \frac{V_{nl} - V_{rated}}{V_{rated}} \cdot 100\% \quad \%VR = \frac{125.833 \text{ V} - 120 \text{ V}}{120 \text{ V}} \cdot 100\% = 4.86\%$$

24

End Lesson 8: Induced Voltage in Practical dc Machines

ET 332a

Dc Motors, Generators and Energy Conversion Devices

25