 


Lesson 8\_et438b.pptx

## LESSON 8: ANALOG SIGNAL CONVERSION

ET 438b Sequential Control and Data Acquisition  
Department of Technology



Lesson 8\_et438b.pptx

### LEARNING OBJECTIVES


After this presentation you will be able to:

- Determine the resolution and accuracy of a digitized analog signal.
- Explain how digital-to-analog converts operate
- Explain how commonly used analog-to-digital converts operate
- Compare and contrast the characteristics several commonly used analog-to-digital converters.

2

## ANALOG SIGNAL CONVERSION

### Two Problems

 

Lesson 8, et438b.pptx

Number of bits in digital signal determines the resolution of the digital signals. Resolution also depends on voltage

3

## RESOLUTION AND ACCURACY OF DIGITIZED SIGNALS


**Resolution** - smallest number that can be measured

**Accuracy** - is the number measured correct
 
### ADC Resolution

The output is a discretized version of the continuous input.

Error determined by the step size of the digital representation



Lesson 8, et438b.pptx

4

## RESOLUTION FORMULAS

Resolution, in terms of full scale voltage of ADC, is equal to value of Least Significant Bit (LSB)

$$V_{LSB} = \frac{V_{fs}}{2^n}$$

Where

$V_{fs}$  = full scale voltage

n = number of bits

$V_{LSB}$  = voltage value of LSB

Finite bit digital conversion introduces quantization errors that range from  $\pm V_{LSB}/2$

Maximum quantization error is

$$Q.E. = \frac{V_{LSB}}{2}$$


Where Q.E. = quantization error

$V_{LSB}$  = voltage value of LSB

5

Lesson 8\_et438b.pptx

## DIGITAL RESOLUTION AND ERROR IN ADC

 

Lesson 8\_et438b.pptx

6

## RESOLUTION FORMULAS

**Percent Resolution-** Based on the number of transitions ( $2^{n-1}$ )

$$\% \text{resolution} = \frac{1}{2^n - 1} \cdot 100\%$$

Where  $n$  = number of bits in digital representation

Lesson 8\_et438b.pptx

**Example 1:** An 8-bit digital system is used to convert an analog signal to digital signal for a data acquisition system. The voltage range for the conversion is 0-10 V. Find the resolution of the system and the value of the least significant bit

$n=8$  so signal converted to 256 different levels.

$V_{fs}=10$  Vdc

$$V_{LSB} = \frac{V_{fs}}{2^n}$$

$$V_{LSB} = \frac{V_{fs}}{2^n} = \frac{10 \text{ V}}{2^8} = \frac{10}{256} = 0.0390625 \text{ V}$$

$$\% \text{resolution} = \frac{1}{2^n - 1} \cdot 100\%$$

$$\% \text{resolution} = \frac{1}{2^8 - 1} \cdot 100\%$$

$$\% \text{resolution} = 0.392\%$$

7

**Example 2:** The 8-bit converter of the previous example is replaced with a 12 bit system. Compute the resolution and the value of the least significant bit.

Signal converted to 4096 different levels  $n = 12$


$$V_{LSB} = \frac{V_{fs}}{2^n} \quad n = 12 \text{ bits} \quad V_{fs} = 10 \text{ Vdc}$$

$$V_{LSB} = \frac{V_{fs}}{2^n} = \frac{10 \text{ V}}{2^{12}} = \frac{10}{4096} = 0.002441 \text{ V}$$

$$\% \text{resolution} = \frac{1}{2^{12} - 1} \cdot 100\%$$

$$\% \text{resolution} = 0.0244\%$$

 Difference between analog value and digital reconstruction is quantizing error




8

Lesson 8\_et438b.pptx

# Digital-to-Analog Conversion

 
## Digital-to-Analog Converter (DAC) Transfer Function



Lesson 8\_ce438b.pptx

## TYPE OF DIGITAL-TO-ANALOG CONVERTERS

### Binary-Weighted Resistor DAC

 


B0, B(n-3), B(n-2), ..., B(n-1) take on values of 1 or 0 depending on the digital output controlling switch

Lesson 8\_ce438b.pptx


## BINARY WEIGHTED DAC EXAMPLE

 **Example:** For the binary-weighted resistor DAC below find the output when the input word is  $1101_2$  V = 10 Vdc,  $R_f = R$


 
## R-2R BINARY LADDER DAC

R-2R Ladder produces binary weighted current values from only 2 resistance values.




### Circuit Analysis

Currents through each 2R value resistor directed to OP AMP or ground by digital switch

Network equivalent resistance is R

## R-2R LADDER ANALYSIS (CONTINUED)

 

$$I_1 = \frac{V_1}{R_1} = \frac{10 \text{ V}}{20 \text{ k}\Omega} = 0.5 \text{ mA} \quad I = I_{in} - I_1 = 1 \text{ mA} - 0.5 \text{ mA} = 0.5 \text{ mA}$$

$$V_2 = V_1 - I \cdot R_2 \Rightarrow V_2 = 10 - 0.5 \text{ mA} \cdot 10 \text{ k}\Omega = 10 - 5 = 5 \text{ V}$$

$$I_2 = \frac{V_2}{R_3} = \frac{5 \text{ V}}{20 \text{ k}\Omega} = 0.25 \text{ mA} \quad I' = I_1 - I_2 = 0.5 \text{ mA} - 0.25 \text{ mA} = 0.25 \text{ mA}$$

$$V_3 = V_2 - I' R_4 \Rightarrow V_3 = 5 - 0.25 \text{ mA} \cdot 10 \text{ k}\Omega = 5 - 2.5 = 2.5 \text{ V}$$

$$I_3 = \frac{V_3}{R_5} = \frac{2.5 \text{ V}}{20 \text{ k}\Omega} = 0.125 \text{ mA} \quad I_4 = \frac{V_3}{R_6} = \frac{2.5 \text{ V}}{20 \text{ k}\Omega} = 0.125 \text{ mA}$$

### Current Values

$$\begin{aligned} I_1 &= 0.5 \text{ mA MSB} \\ I_2 &= 0.25 \text{ mA} \\ I_3 &= 0.125 \text{ mA LSB} \end{aligned}$$

Current values directed to OP AMP summing junction or ground. At summing junction:


$$V_o = -R_f I_T$$

Lesson 8. et438b.pptx

13
 
## R-2R EXAMPLE

Find the output voltage for the R-2R DAC shown below. The digital input is 110<sub>2</sub>.  $R=15\text{k}$ ,  $2R=30\text{k}$  and  $R_f=15\text{k}$ ,  $V_{ref}=5 \text{ Vdc}$



$$I_1 = \frac{I_2}{2} \Rightarrow I_1 = \frac{0.1667 \text{ mA}}{2} = 0.0833 \text{ mA} = 83.33 \mu\text{A}$$

$$I_0 = \frac{I_1}{2} = \frac{0.0833 \text{ mA}}{2} = 0.04166 \text{ mA} = 41.66 \mu\text{A}$$

$$I_T = I_2 + I_1 = 0.1667 \text{ mA} + 0.0833 \text{ mA} = 0.25003 \text{ mA}$$


$$V_o = -I_T R_f = -(0.25003 \text{ mA})(15 \text{ k}\Omega) = -3.75095 \text{ V}$$

Lesson 8. et438b.pptx

14
 
## COMMERCIAL DACS: DAC0800 FAMILY

Devices used in practical designs use integrated R-2R networks and transistor switching. They have TTL compatible inputs.



Design Equations

$$I_{ref} = \frac{V_{ref}}{R_{ref}}$$

$$I_o = I_{ref} \left( \frac{D}{256} \right)$$

D = decimal equivalent of binary input

8-bit binary code converted to 256 levels of  $I_o$ . Full scale value set by reference current. 1 bit change produces change of 1/256 in  $I_o$

$$I_{fs} = \frac{V_{ref}}{R_{ref}} \left( \frac{255}{256} \right)$$

Full scale output


Lesson 8, et438b.pptx

15

## DAC0800 EXAMPLE

Use OP AMP to convert current to voltage. The reference voltage is +10 V dc and the reference resistance is 5 kΩ. The value of  $R_f = 2.5\text{k}\Omega$

Lesson 8, et438b.pptx

 

$$I_{ref} = \frac{V_{ref}}{R_{ref}} = \frac{10\text{ V}}{5\text{ k}\Omega} = 2.0\text{ mA}$$

a.) convert binary to decimal

$$1101_2 = 2^3(1) + 2^2(1) + 2^1(0) + 2^0(1)$$

$$1101_2 = 8 + 4 + 1 = 13$$

$$D = 13$$

$$\text{Find } I_o \quad I_o = I_{ref} \left( \frac{D}{256} \right)$$

$I_o$  enters so negative

- a.) Digital input  $00001101_2$
- b.) Digital input  $10001101_2$

$$I_o = (2.0\text{ mA}) \left[ \frac{13}{256} \right] = 0.1015625\text{ mA} = 101.5625\text{ }\mu\text{A}$$


$$V_o = -(-I_o) \cdot R_f = -(-0.1015625\text{ mA})(2.5\text{ k}\Omega) = 0.253906\text{ V}$$

16
 
## DAC0800 EXAMPLE (CONTINUED)

b.) Digital input  $10001101_2$

$$I_{ref} = \frac{V_{ref}}{R_{ref}} = \frac{10\text{ V}}{5\text{ k}\Omega} = 2.0\text{ mA}$$



b.) convert binary to decimal

$$10001101_2 = 2^7(1) + 2^6(0) + 2^5(0) + 2^4(0) + 2^3(1) + 2^2(1) + 2^1(0) + 2^0(1)$$

$$1101_2 = 128 + 8 + 4 + 1 = 141$$

$$D = 141$$

$I_o$  enters so negative

$$I_o = I_{ref} \left( \frac{D}{256} \right) = (2.0) \cdot \left( \frac{141}{256} \right) = 1.1015626\text{ mA}$$

17

$$V_o = -(-I_o) \cdot R_f = -(-1.1015625\text{ mA})(2.5\text{ k}\Omega) = 2.753906\text{ V}$$

Lesson 8, et438b.pptx

## ANALOG-TO-DIGITAL CONVERSION (ADC)

Converting continuous signals to digital values requires 3 steps

1

Sample analog signal. Nyquist rate or above  
Need a minimum of 2x highest frequency  
Higher rates ease signal reconstruction

2

Hold analog sample while conversion is in progress

3

Convert analog value to digital value (binary)

Lesson 8, et438b.pptx

18

## TYPES OF ANALOG-TO-DIGITAL CONVERTERS

### Integrating

- High Accuracy
- Low Speed
- Low Cost
- Not commonly used in DAQ

### Tracking (Counter Type)

- High Speed in tracking mode
- Slow Conversion times (Some Sub-types)
- Noise Sensitive

### Successive Approximation

- Conversion time independent of input value
- Most commonly used in DAQ applications

19

## TYPES OF ANALOG-TO-DIGITAL CONVERTERS

### “Flash” or Parallel


- Multi-Comparators
- Highest Speed
- High Cost

### Delta/Sigma

- One bit Conversion
- High Resolution
- Ratio of 1-to-0 represent input
- Uses digital filtering

20
 
## COUNTER-TYPE ANALOG-TO-DIGITAL CONVERTER OPERATION




Lesson 8, et438b.pptx

21


- 1.) Input a constant value. Requires a sample and hold circuit.  
(Not Shown)
- 2.) AND gate passes clock signal when point A logic high
- 3.) Counter incremented by signal B
- 4.) DAC output increases as counter output increases
 
## COUNTER-TYPE ANALOG-TO-DIGITAL CONVERTER OPERATION



Lesson 8, et438b.pptx

 - 5.) Counter stops when DAC V exceeds input V



22

## SUCCESSIVE APPROXIMATION ADC

Counter A/D converters conversion time proportional to the input level. Improve conversion speed using a binary search technique.

Lesson 8, et438b.pptx


23

### Procedure


1. Set MSB to 1
2. Test input,  $V_{in}$ , against DAC output,  $V_{DAC}$
3. If  $V_{DAC} > V_{in}$ , reset bit to 0, else bit = 1 ( $V_{DAC} < V_{in}$ )
4. Move to next bit and repeat steps 1 - 3

The input is converted to digital value in n steps, where n = the number of bits in digital representation

## SUCCESSIVE APPROXIMATION ADCS

 

Successive Approx.  
Register

 

Lesson 8, et438b.pptx

24

## SUCCESSIVE APPROXIMATION ADC

**Example:** An 8-bit successive approximation ADC has an input voltage of 13.478 V. The ADC full scale input voltage is 20 V. Use the successive approximation algorithm given previously to determine the binary value. Assuming that each bit test takes a single clock cycle, determine the maximum conversion time for the ADC if it is clocked at 4.77 MHz.

Lesson 8 et438b.pptx

25

### Example Solution

26

Lesson 8 et438b.pptx

Voltage Weight	10.0	5.0	2.5	1.25	0.625	0.3125	0.15625	0.078125	Cycle
Bit	D7	D6	D5	D4	D3	D2	D1	D0	
Set D7	0	0	0	0	0	0	0	0	1
Set D6	1	0	0	0	0	0	0	0	2
Set D5	1	0	0	0	0	0	0	0	3
Set D4	1	0	1	0	0	0	0	0	4
Set D3	1	0	1	0	0	0	0	0	5
Set D2	1	0	1	0	1	0	0	0	6
Set D1	1	0	1	0	1	1	0	0	7
Set D0	1	0	1	0	1	1	1	0	8
	1	1	1	1	1	1	1	1	

1.  $10 < 13.478$  bit remains set5.  $10 + 2.5 + 0.625 < 13.478$  bit remains set2.  $10 + 5 > 13.478$  reset bit6.  $10 + 2.5 + 0.625 + 0.3125 < 13.478$  bit remains set3.  $10 + 2.5 < 13.478$  bit remains set7.  $10 + 2.5 + 0.625 + 0.3125 + 0.15625 > 13.478$  bit reset4.  $10 + 2.5 + 1.25 > 13.478$  reset bit8.  $10 + 2.5 + 0.625 + 0.3125 + 0.15625 + 0.078125 > 13.478$  bit reset

### Example Solution (Continued)

#### Summary Results

Final binary value:  $B=10101100_2$

Final voltage:  $10+2.5+0.625+0.3125 = 13.4375 \text{ V}$

Quantization Error voltage:  $V_{QE}=13.478 \text{ V}-13.4375 \text{ V} = 0.0405 \text{ V}$   
or 40.5 mV

#### Determine conversion time

Define  $T_c$  as clock period =  $1/f_c$  Where  $f_c$  = ADC Clock = 4.77 MHz

$$T_c = \frac{1}{f_c} = \frac{1}{4.77 \times 10^6 \text{ Hz}} = 2.096 \times 10^{-7} \text{ S} = 0.2096 \mu\text{S}$$

All conversions take 8 clock cycles so maximum conversion time is  $8 \cdot T_c$

$$T_{con} = 8 \cdot T_c = 8 \cdot (0.2096 \mu\text{S}) = \underline{\underline{1.667 \mu\text{S}}} \text{ Ans}$$

27

### Example Solution (Continued)

What is the highest frequency that the system can convert without folding or aliasing. Assume that the sample and hold time is zero.

Define the maximum conversion rate frequency,  $f_{con(max)}$

$$f_{con(max)} = \frac{1}{T_{con}} = \frac{1}{1.667 \times 10^{-6} \text{ S}} = 596,250 \text{ Hz}$$

Signals must be sampled at least twice per period (Nyquist rate)


$$2 \cdot f_{in} = f_{con(max)}$$

$$f_{in} = \frac{f_{con(max)}}{2} = \frac{596,250 \text{ Hz}}{2} = 298,125 \text{ Hz} \quad \text{Ans}$$

28


 
## END LESSON 8: ANALOG SIGNAL CONVERSION



29

ET 438b Sequential Control and Data Acquisition  
Department of Technology

