

ET 332a

Dc Motors, Generators and Energy Conversion Devices

## LESSON 12 SHUNT CONNECTED DC MOTORS

1

## LEARNING OBJECTIVES


After this presentation you will be able to:

- Draw the circuit model of a shunt motor and label all parts correctly
- Use the shunt motor equations to perform calculations on shunt dc motor operation
- Draw and explain how the shunt motor torque speed characteristic affects its operation.

2
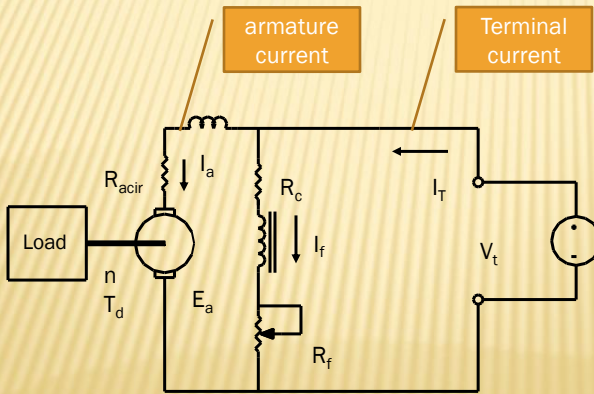
# SHUNT CONNECTED DC MOTORS

Field current supplied from the same source as armature. Field current constant if not modified by rheostat.



Motor circuit model schematic

Motor Model Equations

$$I_a = I_T - I_f$$

$$E_a = V_T - I_a \cdot R_{acir}$$


Motor Speed

$$n = \frac{E_a}{\Phi_p \cdot k_G} \quad \Phi_p \cdot k_G = K_e$$

$$n = \frac{V_T - I_a \cdot R_{acir}}{\Phi_p \cdot k_G}$$

Speed proportional to  $E_a$

# SHUNT CONNECTED DC MOTORS

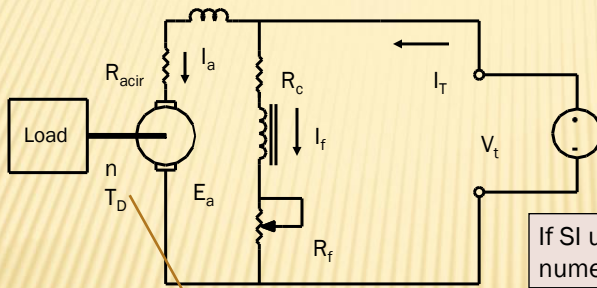

Developed Torque

Developed Torque

$$T_D = K_T \cdot I_a$$

Torque proportional to armature current

If SI units are used,  $K_e = K_T$  numerically


Power balance in the armature

$$P_e = P_{em}$$

$$E_a \cdot I_a = T_D \cdot \omega$$

Lesson 12 332a.pptx
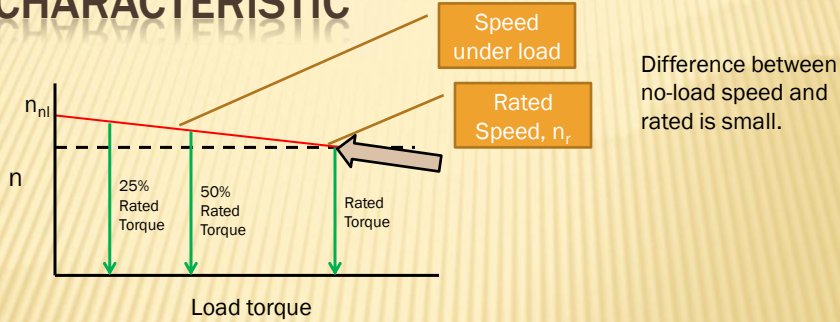
## SHUNT MOTOR TORQUE-SPEED CHARACTERISTIC




Shunt motor gives almost constant speed for over wide range of mechanical load torques.

5

Lesson 12 332a.pptx

## SHUNT MOTOR SPEED EXAMPLE 12-1

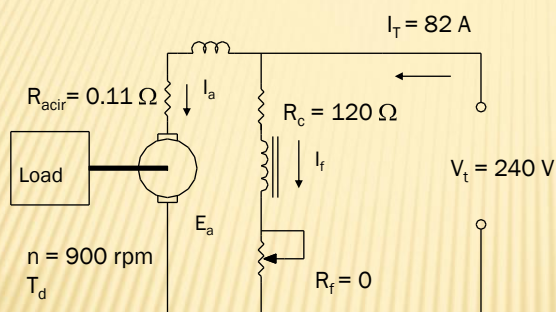

Find the motor terminal current and the motor speed when the developed torque load is increased by 50% from the initial conditions given.

Calculate the speed regulation for the change in load conditions given above

6

## EXAMPLE 12-1 SOLUTION (1)

Find  $I_a$  from the terminal current and the field current

$$I_T = 82 \text{ A}$$

$$I_a = I_T - I_f \quad I_f = \frac{V_T}{R_c} = \frac{240 \text{ V}}{120 \Omega} = 2 \text{ A}$$

$$I_a = 82 - 2 \text{ A} = 80 \text{ A}$$

Find  $E_a$

$$E_a = V_T - I_a R_{acir} \quad R_{acir} = 0.11 \Omega$$

$$E_a = 240 \text{ V} - (80 \text{ A})(0.11 \Omega)$$

$$E_a = 231.2 \text{ V}$$

Electric power developed

$$P_e = E_a I_a = (231.2 \text{ V})(80 \text{ A}) = 18,496 \text{ W}$$

7

## EXAMPLE 12-1 SOLUTION (2)

Electric power equals electromechanical power in the armature

$$P_{em} = P_e \Rightarrow T_d \omega = E_a I_a$$

$$T_d = \frac{E_a I_a}{\omega} = \frac{P_e}{\omega}$$

$$\omega = \text{speed in rad/sec} \quad n = 900 \text{ RPM}$$

$$\omega = \left[ \frac{2\pi}{60} \right] n \quad \omega = \left[ \frac{2\pi}{60} \right] 900 \text{ RPM}$$

$$\omega = 94.25 \text{ rad/s}$$

$$T_d = \frac{18,496 \text{ W}}{94.25 \text{ rad/s}}$$

$$T_d = 196.24 \text{ rad/s}$$

Torque at initial  
operating point

Compute 50% Torque Increase

$$T_{d50} = T_d + T_d \left[ \frac{50\%}{100\%} \right]$$

$$T_{d50} = 196.24 + 196.24 \left[ \frac{50\%}{100\%} \right]$$

$$T_{d50} = 294.4 \text{ N}\cdot\text{m}$$

8

## EXAMPLE 12-1 SOLUTION (3)

Compute the torque constant to find the new armature current

$$K_T = \frac{196.24 \text{ N}\cdot\text{m}}{80 \text{ A}} = 2.452 \text{ N}\cdot\text{m}/\text{A}$$

$$T_d = K_T I_{ad} \quad K_T \text{ IS CONSTANT} \\ \text{as } T_d \text{ increases}$$

$$T_{d50} = K_T I_{a50}$$

$$\frac{T_{d50}}{K_T} = I_{a50}$$

Compute  $I_{a50}$  using  $K_T$  and  $T_{d50}$

$$\frac{T_{d50}}{K_T} = I_{a50} \Rightarrow \frac{294.9 \text{ N}\cdot\text{m}}{2.453 \text{ N}\cdot\text{m}/\text{A}} = 120 \text{ A}$$

Terminal current, add  $I_f$  to  $I_{a50}$

$$I_T = I_a + I_f = 120 \text{ A} + 2 \text{ A} = \boxed{122 \text{ A}}$$

9

## EXAMPLE 12-1 SOLUTION (4)

Find new speed

$$\omega = \frac{V_T - I_a R_{acir}}{K_e}$$

Remember  $K_e = K_T$  numerically in SI unit. Constant  $I_f$  means  $K_e$  is constant from load 1 to load 2

new load motor speed  
 $I_{a50} = 120 \text{ A}$  omit  $I_f$

$K_e = K_T = 2.453 \text{ V}/\text{rad}/\text{s}$   
 use different units

$$\omega_{50} = \frac{V_T - I_{a50} R_{acir}}{K_e}$$

$$\omega_{50} = \frac{295 - (120 \text{ A})(0.115 \Omega)}{2.453 \text{ V}/\text{rad}/\text{s}}$$

$\omega_{50} = 92.958 \text{ rad}/\text{s}$   
 Convert to RPM

10

## EXAMPLE 12-1 SOLUTION (5)

Convert radians/second to rpm to compare with initial speed of 900 rpm

$$n_{50} = \omega_{50} \left( \frac{60}{2\pi} \right)$$

$$92.458 \left[ \frac{60}{2\pi} \right] = n_{50}$$

$$882.91 \text{ rpm} = n_{50}$$

Calculate percentage speed change for a 50% increase in load developed torque. Take 900 rpm as the base speed,  $n_b$ .

$$\% \Delta n = \frac{n_b - n_{50}}{n_b} \times 100\% = \frac{900 - 882.91}{900} \times 100\%$$

$$\% \Delta n = 1.9\% \quad \text{speed change for}$$

$$50\% \text{ Torque increase}$$

Almost constant speed over wide load torque range. Shunt motor considered constant speed motor

11

ET 332a

Dc Motors, Generators and Energy Conversion Devices

## END LESSON 12

12